

# AN923: EFR32 sub-GHz Matching Guide



The EFR32 family of RFICs includes chip variants that provide 2.4 GHz-only operation, sub-GHz-only operation, or dual-band (2.4 GHz and sub-GHz) operation. This application note provides a description of the RF matching for those EFR32 chip variants that provide sub-GHz operation.

**Note:** This document does *not* address the matching procedure for the 2.4 GHz path. The 2.4 GHz matching procedure is described in “AN930: EFR32 2.4 GHz Matching Guide”.

## KEY POINTS

- Provides an overview of matching procedure
- Specifically discusses design procedures for the lowpass filter, balun, and impedance transformation network
- Shows how to apply the information provided

## 1. Introduction

The EFR32 family of RFICs includes chip variants that provide 2.4 GHz-only operation, sub-GHz-only operation, or dual-band (2.4 GHz and sub-GHz) operation. This application note provides a description of the RF matching for those EFR32 chip variants that provide sub-GHz operation.

**Note:** This document does *not* address the matching procedure for the 2.4 GHz path. The 2.4 GHz matching procedure is described in "AN930: EFR32 2.4 GHz Matching Guide".

The layout design of the match is critical to achieve the targeted power and efficiency. This is especially true for the RX path, which can be easily detuned by the PCB parasitics. Because of this, Silicon Labs suggests copying the RF part of the reference PCB design, or if it is not possible, applying the layout design rules and guidelines described in "AN928: EFR32 Layout Design Guide".

The matching effort strives to simultaneously achieve several goals:

- Provide for tying together the TX and RX signal paths, external to the RFIC.
- Provide the desired nominal TX output power level (measured at the connector to the antenna / load).
- Obtain this nominal TX output power at the nominal supply voltage.
- Provide optimal RX Sensitivity.
- Minimize current consumption (i.e., maximize efficiency).
- Comply with regulatory specifications for spurious emissions.

The matching procedures outlined in this document will help achieve the goals listed above.


[Table 3.1 Summary of Matching Component Values vs. Frequency \(CLNA = 1.0 pF\) on page 21](#) and [Table 3.2 Summary of Matching Component Values vs. Frequency \(CLNA = 1.25 pF\) on page 22](#) are provided for users more interested in quickly obtaining matching component values than in the methodology used to develop the matching network.

[Table 3.3 Summary of Matching RF performance in TX mode \(CLNA = 1.0 pF\) on page 22](#) summarizes the RF performance of the matches used in Silicon Laboratories reference designs.

## 2. Matching Procedure

### 2.1 Overview


The sub-GHz LNA and PA circuits in EFR32 RFICs are fully differential and are not tied together inside the chip. As a result, a total of four pins are required on the RFIC to provide access to the LNA and PA circuits: SUBGRF\_OP/ON for the TX output, and SUBGRF\_IP/IN for the RX input. These four pins are adjacently located, as shown in the figure below, regardless of chip variant. The RF matching circuit must provide for connecting the TX and RX signal paths together, external to the RFIC.

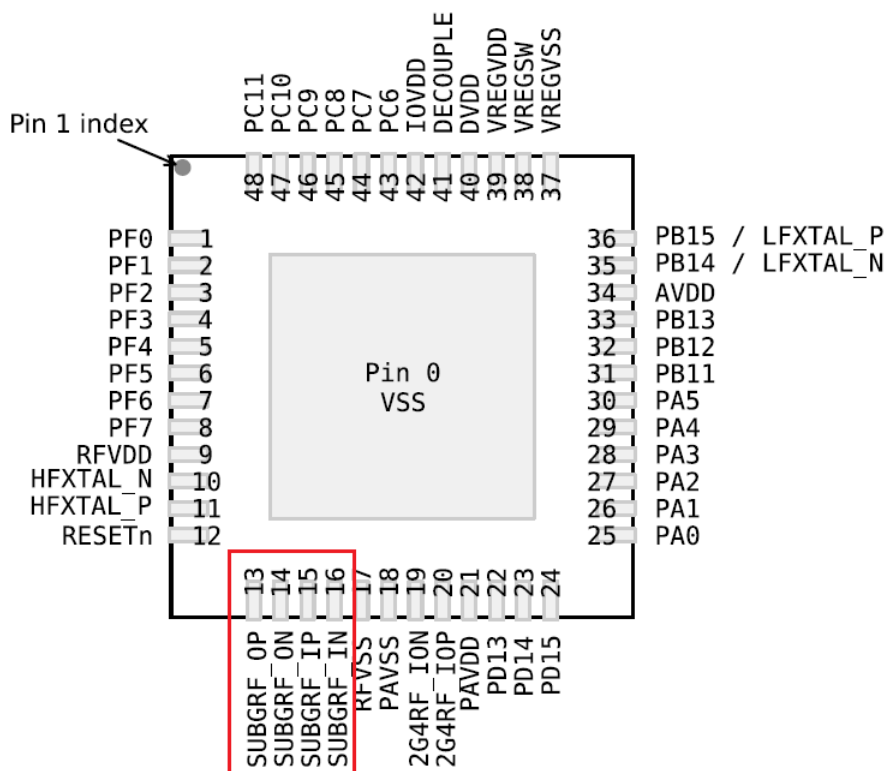

**Figure 2.1. Example Pin Locations of sub-GHz TX and RX Functions**

The general topology of the sub-GHz RF matching network is shown in the figure below. The RF matching network consists of the following blocks:

- A lowpass filter section (for suppression of harmonics and spurious emissions in TX mode).
- A balun (to provide a single-ended to differential conversion function).
- An impedance transformation section (to present the correct impedances to the TX and RX pins of the RFIC).

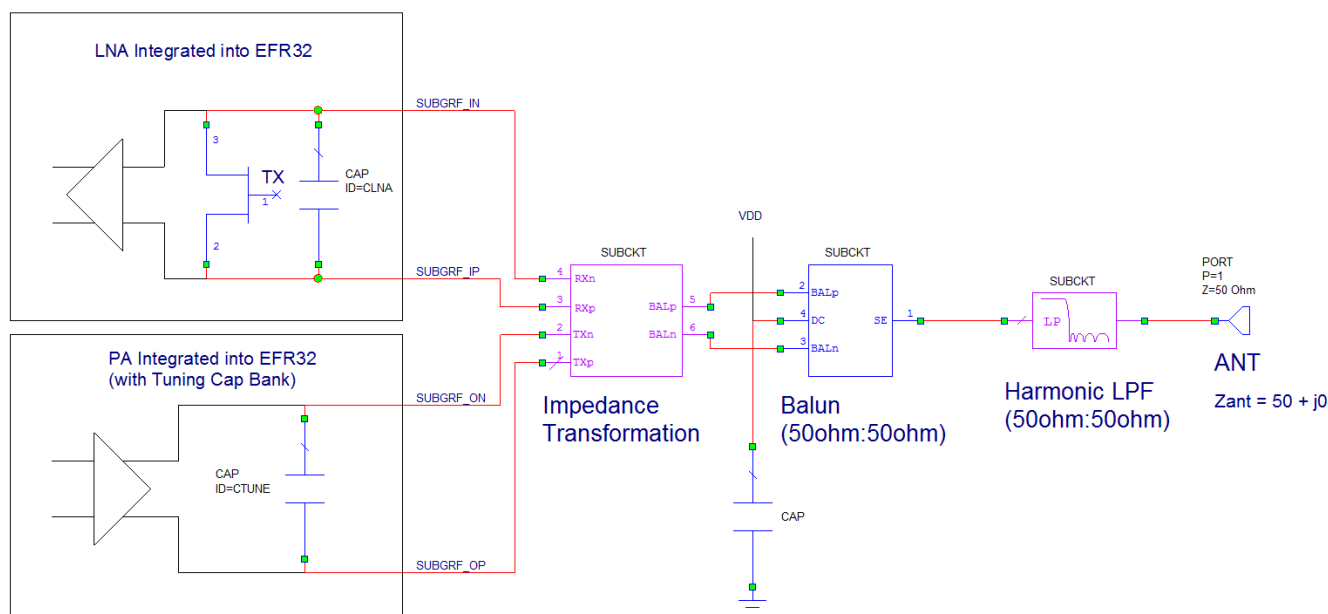

**Figure 2.2. General Topology of sub-GHz RF Match**

The TX pins of the RFIC (SUBGRF\_OP/ON) must be supplied with the  $V_{DD}$  supply voltage. Many commercially available baluns provide a center tap on their balanced port through which the DC voltage may be applied, as shown in the figure above. If the selected balun does not provide such a center tap, it is necessary to supply the DC voltage to the TX pins through a pair of high-value DC pull-up inductors.

The circuit block that provides the impedance transformation function is the “interesting” part of the match, and will receive the most discussion within this application note. This circuit block is also where the TX and RX signal paths are tied together.

## 2.2 Lowpass Filter

The lowpass filter network is designed to attenuate the TX harmonics and spurious emissions below the level required to meet applicable regulatory standards (e.g., FCC, ETSI, or ARIB).


It is difficult for Silicon Labs to recommend one single lowpass filter design that is appropriate for all customers, as customers may operate at significantly different TX power levels as well as under widely differing regulatory standards and harmonic requirements. Also, the radiation efficiency of the antenna selected by the customer is not known in advance. These factors make it difficult for Silicon Labs to conclusively state the required filter attenuation characteristics.

The selected filter type (e.g., Butterworth, Chebyshev, Elliptic) is not a mandatory design constraint. If the selected filter provides acceptable attenuation of the harmonic signal energy and reasonable insertion loss, it is a “good” filter. Silicon Labs typically uses Chebyshev lowpass filter networks with small (0.25 dB to 0.5 dB) passband amplitude ripple as a good trade-off between flat passband response and rate of attenuation in the stopband. The filter design should, however, be designed for a 1:1 impedance transformation (i.e., 50  $\Omega$  input and 50  $\Omega$  output impedance). This will greatly simplify the subsequent connection of the additional matching network blocks (i.e., balun and impedance transformation network).

Filter component values may be obtained by usual design methods, such as use of Filter Design CAD software or tables of normalized filter values scaled to the desired frequency of operation, and will not be further discussed here. However, Silicon Labs has developed matching networks across a wide range of frequencies, supporting a range of TX output power levels. The measured results from those matching exercises lead to the following general statements:

- An application with +20 dBm TX output power level will likely need a 5<sup>th</sup>-order or 7<sup>th</sup>-order lowpass filter, depending upon the stringency of the applicable regulatory standard.
- An application with +10 dBm (or less) TX output power level will only need a 3<sup>rd</sup>-order lowpass filter.
- An application with +14 dBm TX output power level will need either a 3<sup>rd</sup>-order or 5<sup>th</sup>-order lowpass filter, depending upon the limits of the applicable standards.

The topology of the lowpass filter(s) used by Silicon Labs is shown in the figure below.

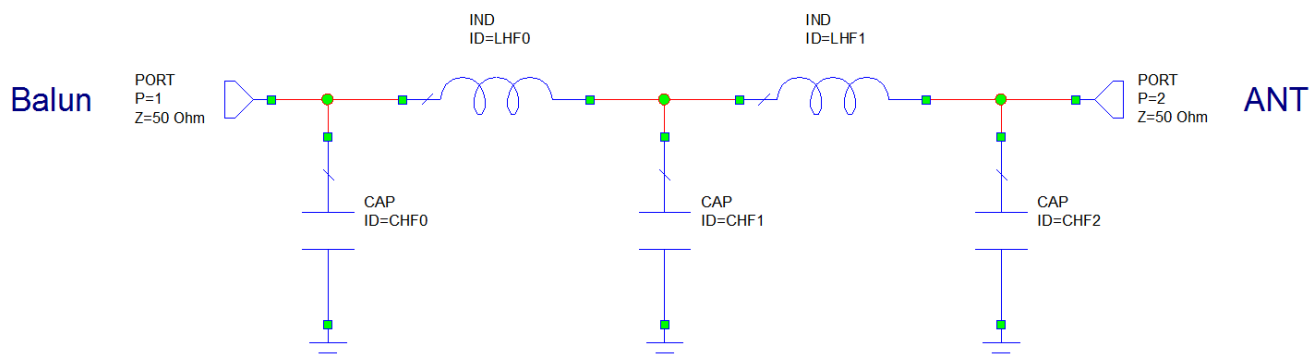

**Figure 2.3. Lowpass Filter Topology**

A summary of lowpass filters developed for use in Silicon Labs' reference designs is shown in the table below. All filters summarized in this table are symmetrical designs (due to the 1:1 impedance transformation ratio). In those few instances where the component values are not perfectly symmetrical (i.e., CHF0  $\neq$  CHF2 or LHF0  $\neq$  LHF1), the reason is that the design has been slightly adjusted to compensate for parasitic effects of the actual board layout.

**Table 2.1. Lowpass Filter Component Values vs. Frequency**

Freq Band	Order	CHF0	LHF0	CHF1	LHF1	CHF2	LHF2	CHF3
169 MHz	N = 3	18 pF	47 nH	18 pF	N/A	N/A	N/A	N/A
	N = 5	20 pF	56 nH	33 pF	56 nH	20 pF	N/A	N/A
	N = 7	15 pF	51 nH	33 pF	56 nH	33 pF	51 nH	15 pF
315 MHz	N = 3	8.2 pF	24 nH	8.2 pF	N/A	N/A	N/A	N/A
	N = 5	8.2 pF	30 nH	15 pF	30 nH	8.2pF	N/A	N/A
	N = 7	6.8 pF	30 nH	15 pF	36 nH	15 pF	30 nH	6.8 pF
434 MHz	N = 3	6.8 pF	18 nH	6.8 pF	N/A	N/A	N/A	N/A
	N = 5	6.2 pF	24 nH	11 pF	24 nH	5.6pF	N/A	N/A
490 MHz	N = 3	5.6 pF	15 nH	5.6 pF	N/A	N/A	N/A	N/A
	N = 5	6.2 pF	22 nH	10 pF	22 nH	6.2 pF	N/A	N/A
868 MHz	N = 3	3.9 pF	9.1 nH	3.9 pF	N/A	N/A	N/A	N/A
	N = 5	3.0 pF	11 nH	5.6 pF	11 nH	3.0 pF	N/A	N/A
915 MHz	N = 3	3.6 pF	9.1 nH	3.6 pF	N/A	N/A	N/A	N/A
	N = 5	3.3 pF	10 nH	5.6 pF	10 nH	3.3 pF	N/A	N/A
950 MHz	N = 3	3.3 pF	8.7 nH	3.3 pF	N/A	N/A	N/A	N/A
	N = 5	3.3 pF	9.1 nH	5.6 pF	9.1 nH	3.3 pF	N/A	N/A

The inductors used in Silicon Labs reference designs are currently wire-wound surface mount inductors, such as the Murata LQW15A or LQW18A series, or the CoilCraft 0402CS, 0402HP, 0603CS, or 0603HP series. Wire-wound inductors provide the best performance, but are more expensive. It is possible to use a cheaper series of inductors (i.e., multi-layer inductors such as the Murata LQG15HS series), however, there will be some slight increase in insertion loss that will result in a decrease in TX output power and/or a degradation in RX sensitivity. This degradation in performance is small, typically less than 0.5 dB.

For informational purposes, the frequency response of a typical 5<sup>th</sup>-order lowpass filter using wire-wound inductors is shown in the figure below.

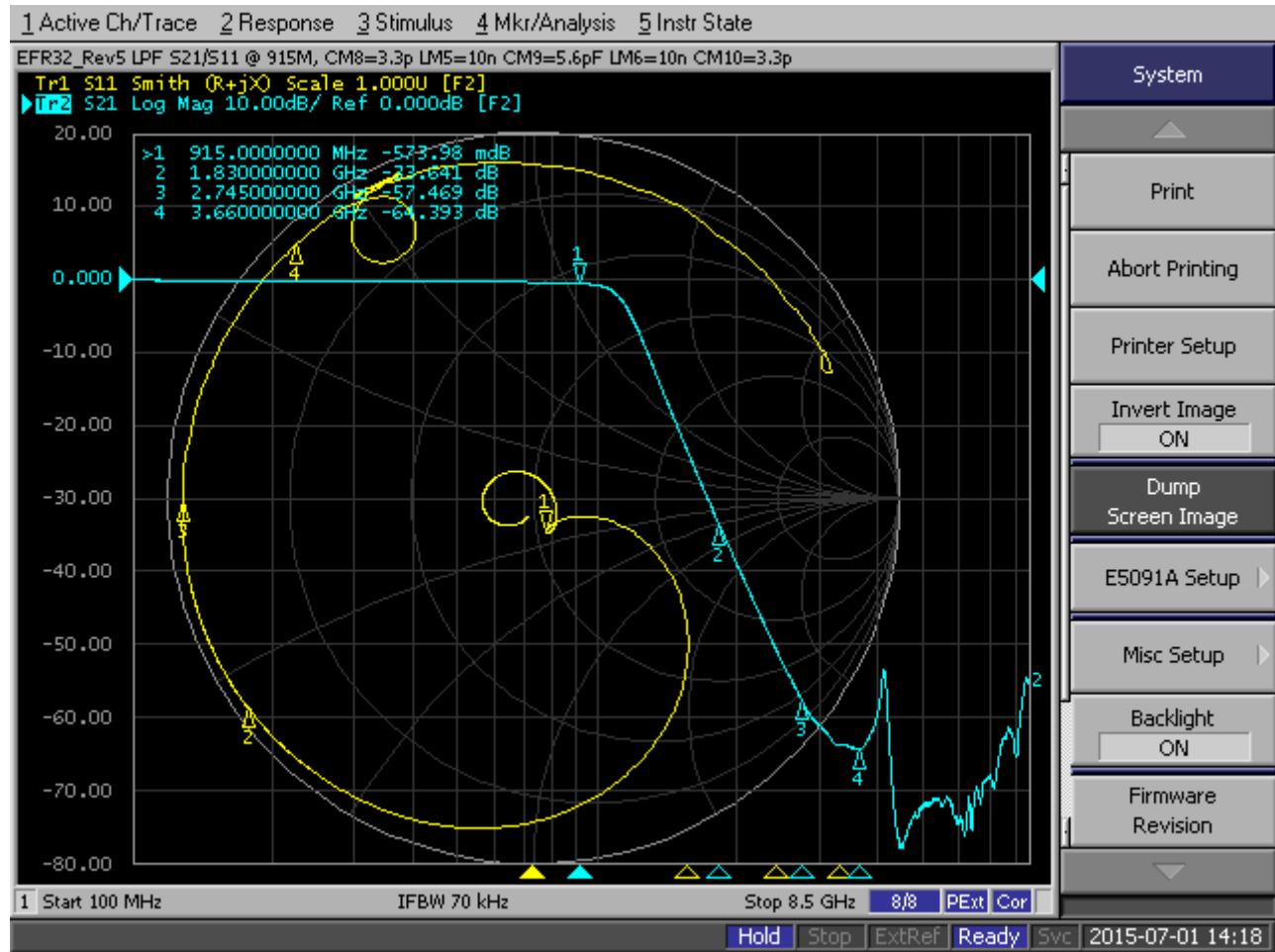


Figure 2.4. Typical Lowpass Filter Frequency Response (915 M, N = 5)


## 2.3 Balun

The balun is selected to provide a single-ended to differential conversion function with minimal insertion loss over the frequency band of interest. As mentioned previously, it is also highly desirable for the balun to provide a center tap through which DC voltage is supplied to the TX output pins.

Silicon Labs currently uses the 0900BL15C050 balun from Johanson Technology for applications within the 868 MHz and 915 MHz frequency bands, and the ATB2012\_50011 balun from TDK for applications within all frequency bands from 169 MHz to 490 MHz. The TDK balun does not provide a center tap and thus it is necessary to supply the  $V_{DD}$  supply voltage to the TX output pins through a pair of high-value DC pull-up inductors.

These baluns selected by Silicon Labs are 50  $\Omega$ :50  $\Omega$  baluns. As shown in [Figure 2.2 General Topology of sub-GHz RF Match on page 3](#), the balun is followed by a circuit block that provides an impedance transformation function. While it may prove possible to select a balun that provides a different impedance transformation ratio (e.g., 50  $\Omega$ :125  $\Omega$ ), thus simplifying the subsequent impedance transformation block, Silicon Labs has not yet investigated this matching approach.

The typical combined performance of a balun and 5<sup>th</sup>-order lowpass filter is shown in the figure below, for informational purposes. This plot depicts the typical insertion loss from the ANT port to the differential port of the balun.

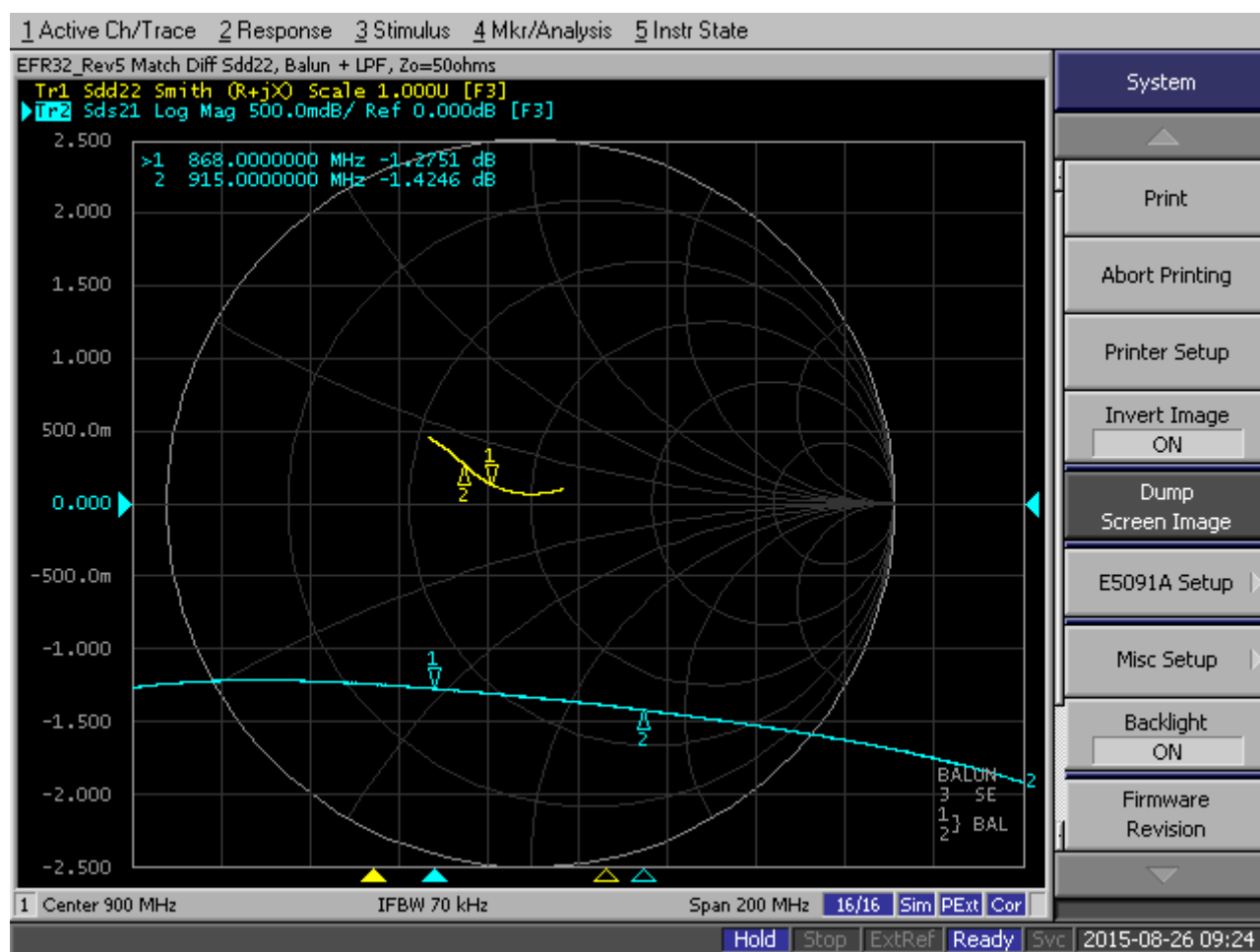


**Figure 2.5. Typical Performance through LPF + Balun (915 MHz, N = 5, 0900BL15C050 Balun)**



## 2.4 Impedance Transformation and TX/RX Tie

The circuit block that provides the impedance transformation and TX/RX tie functions is the most complex part of the match. The general topology of this block (and how it interconnects to the LPF and balun) is shown in the figure below.

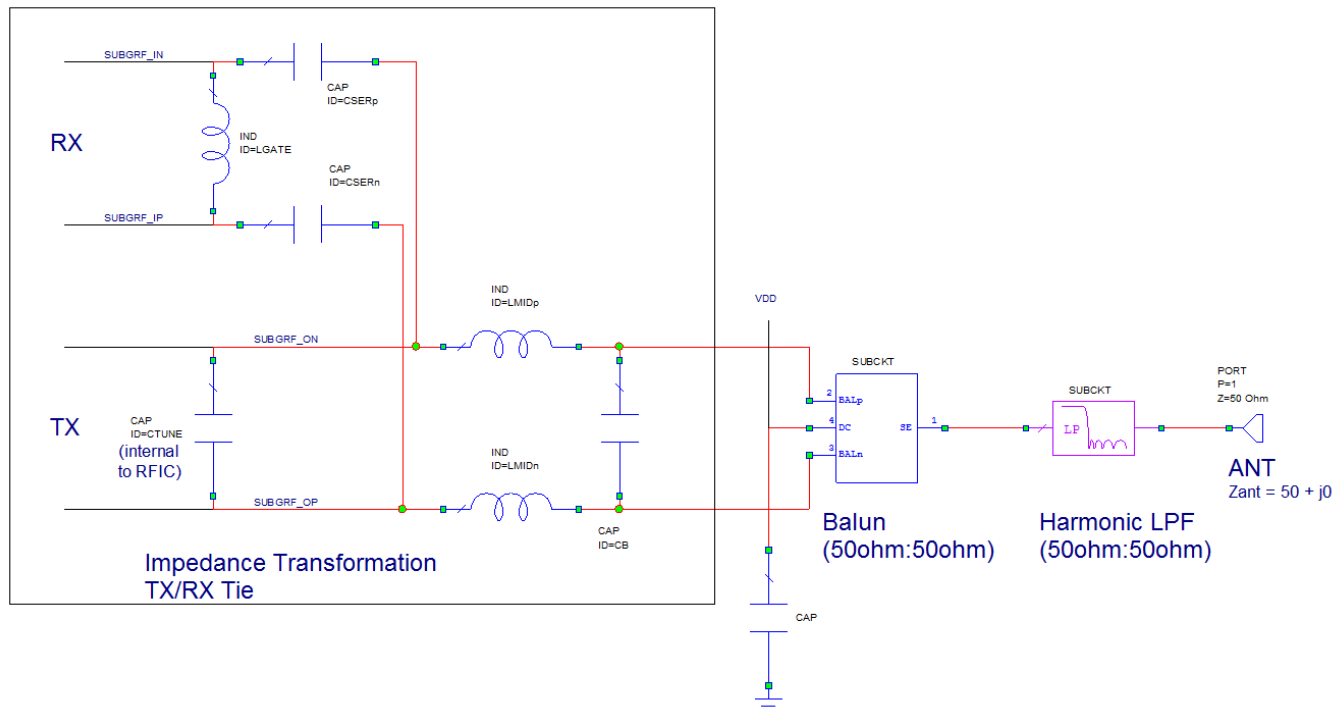

**Figure 2.6. Impedance Transformation Block Topology**

The RX match interacts weakly with the TX path, and thus the recommended design approach is to construct the match for the TX path *first*, followed by the addition of the RX match. As a result, the TX match is discussed first.

## 2.4.1 TX Signal Path and Match

The sub-GHz PA in EFR32 chips uses a Class AB design. The maximum available TX output power (for a given chip variant) is a function of the  $V_{DD}$  voltage supplied to the TX output pins and of the differential load impedance presented to the TX output pins. In a very simplistic sense,

$$P_{OUT\_DIFF} = 2 * P_{OUT\_SE} = 2 * \frac{(0.707 * V_{SWING\_PK\_SE})^2}{R_{LOA\_D\_SE}} = \frac{V_{SWING\_PK\_SE}^2}{R_{LOA\_D\_SE}} \approx \frac{V_{DD}^2}{R_{LOA\_D\_SE}}$$

Equation 1

The task of the designer is to construct the impedance transformation block to present a desired differential load impedance to the output of the PA circuit, given knowledge of the target  $V_{DD}$  supply voltage. Silicon Labs states (without proof presented here) that the following differential load impedances are appropriate for obtaining the listed maximum output powers, for the specified values of  $V_{DD}$  supply voltage.

Table 2.2. Differential PA Load Impedance vs Output Power and VDD


$P_{OUT}$	$V_{DD}$	$R_{LOAD\_DIFF}$
+20 dBm	3.3 V	100 to 125 $\Omega$
+17 dBm	3.3 V	170 $\Omega$
+14 dBm	1.8 V	100 to 125 $\Omega$
+13 dBm	1.8 V	170 $\Omega$
+10 dBm	1.7 V	220 $\Omega$
0 dBm	1.7 V	330 $\Omega$

From the values listed in the table above, it is apparent that one common RF match may (potentially) be used to obtain different output power levels, simply by changing the  $V_{DD}$  voltage supplied to the TX output pins. Although not shown in the table, it is often possible to obtain different output power levels for the same  $V_{DD}$  supply voltage, by changing the differential load impedance presented to the PA. For example, the table above shows that it is possible to obtain +14 dBm from the chip for  $V_{DD} = 1.8$  V and a differential load impedance of 100 to 125  $\Omega$ . It is also possible to obtain +14 dBm from the chip for  $V_{DD} = 3.3$  V and a differential load impedance of ~330  $\Omega$ . The PA current consumption from the 3.3 V supply will be less than the PA current consumption from the 1.8 V supply. However, the EFR32 family of chips provide for an on-chip DCDC Converter, and it is assumed that the 1.8 V (or 1.7 V) PA supply voltage will be obtained from the output of the DC-DC Converter, thus gaining the current efficiency of the converter (i.e., converting  $V_{BATT} = 3.3$  V to  $V_{DD} = 1.8$  V). In most cases, overall chip current consumption is minimized by using the DC-DC Converter as the voltage source for the PA for all applications with TX output power  $\leq +14$  dBm. Moreover, with the DCDC the output power level is stable and immune against  $V_{DD}$  variations.

The output power levels shown in the table above are maximum power levels. For any given match and  $V_{DD}$  supply voltage, the TX output power can be reduced to a less-than-maximum value through the `SetPower(x)` Rail API command. The effect of such an API command is to reduce the number of enabled fingers in the output device(s), thus reducing the bias current and voltage swing across the presented differential load impedance. The designer does not have direct control over the number of enabled fingers of the output device(s), instead the `SetPower(x)` command adjusts the power level nearly to x dBm if the Silicon Labs reference matching designs given in [Table 3.1 Summary of Matching Component Values vs. Frequency \(CLNA = 1.0 pF\) on page 21](#) are used with 125  $\Omega$  termination impedance and the  $V_{DD}$  is 3.3 V. For the cases where the PA is fed from 1.8 V generated by the internal DCDC, the Radio Configurator window should be used in the Simplicity Studio to adjust the `SetPower(x)` Rail API command to the reduced power levels. In this case the maximum power is around 14 to 15 dBm, as shown in [Table 2.2 Differential PA Load Impedance vs Output Power and VDD on page 9](#). With different matching impedances and with different  $V_{DD}$  values, the `SetPower(x)` command yields a power level, which deviates from x dBm.

The TX path of the impedance transformation network is shown in the figure below. It is clear that this network is a fully-differential PI-network (i.e., shunt-C, series-L, shunt-C). So it is the task of the designer to select values for CB, LMID, and CTUNE to transform 50  $\Omega$  (the impedance seen looking back into the balun and lowpass filter) into the desired differential TX load impedance, as listed in [Table 2.2 Differential PA Load Impedance vs Output Power and VDD on page 9](#). This design task is readily accomplished with the aid of a Smith Chart or simple impedance matching application.

There are two items that present minor complications to this design task. First, one of the components of the PI-network is an adjustable capacitor bank (CTUNE, adjustable from ~2 to 7 pF) that is integrated into the RFIC. The designer does not have direct control over the value of this CTUNE capacitor. Instead, the value of CTUNE is set by the API and chip firmware for a value appropriate to support Silicon Labs' reference designs for a particular output power level and  $V_{DD}$  supply voltage. For applications at lower frequencies ( $\leq 390$  MHz), the available adjustment range of CTUNE may not be sufficient to properly tune the PI-network match. In such cases, it may be necessary to augment the value of CTUNE by the addition of external discrete parallel capacitors to GND from the TX pins. Second, board layout parasitics can significantly modify the discrete component values required to accomplish a desired impedance transformation. For example, the series inductance of the PCB traces may provide a significant portion of the required value of the LMID inductors. This series trace inductance should not be ignored or discounted, and may result in use of a lower value inductor for LMID than that predicted by Smith Chart matching calculations.

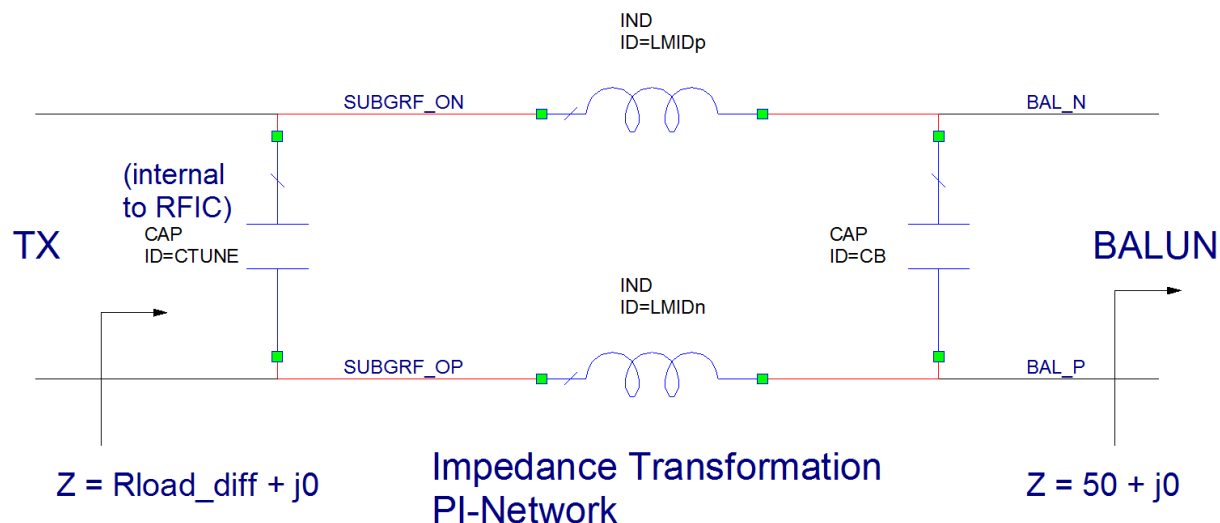

**Figure 2.7. TX Impedance Transformation Network**

The figure below shows a possible simplified matching process on Smith chart where one half of the differential PI network is matched between the half of the differential impedances i.e. between  $50/2 = 25 \Omega$  and  $125/2 = \sim 63 \Omega$ . This example applies ideal reactances. As mentioned above, with real SMD components and PCB parasitics the element values may differ significantly from the ideal values.

In the figure below, the half pi network uses 6.5 pF and 8.7 pF shunt capacitors. In the doubled differential network, where two halves are unified, the half of the shunt capacitor values are used i.e. 3.25pF and ~4.3pF. The resulted differential matching component values are shown in [Figure 2.9 TX Match for Zload = 125  \$\Omega\$  at 915 MHz on page 11](#). It presents a differential load impedance of ~125  $\Omega$  to the PA output, while shows 50  $\Omega$  differential impedance for the balun at an operating frequency of 915 MHz. This solution is not unique; there are many possible combinations of CB-LMID-CTUNE that will transform 50  $\Omega$  to 125  $\Omega$ . However, this solution results in reasonable component values, using readily-available standard 5% tolerance values, with reasonable circuit Q-factor.

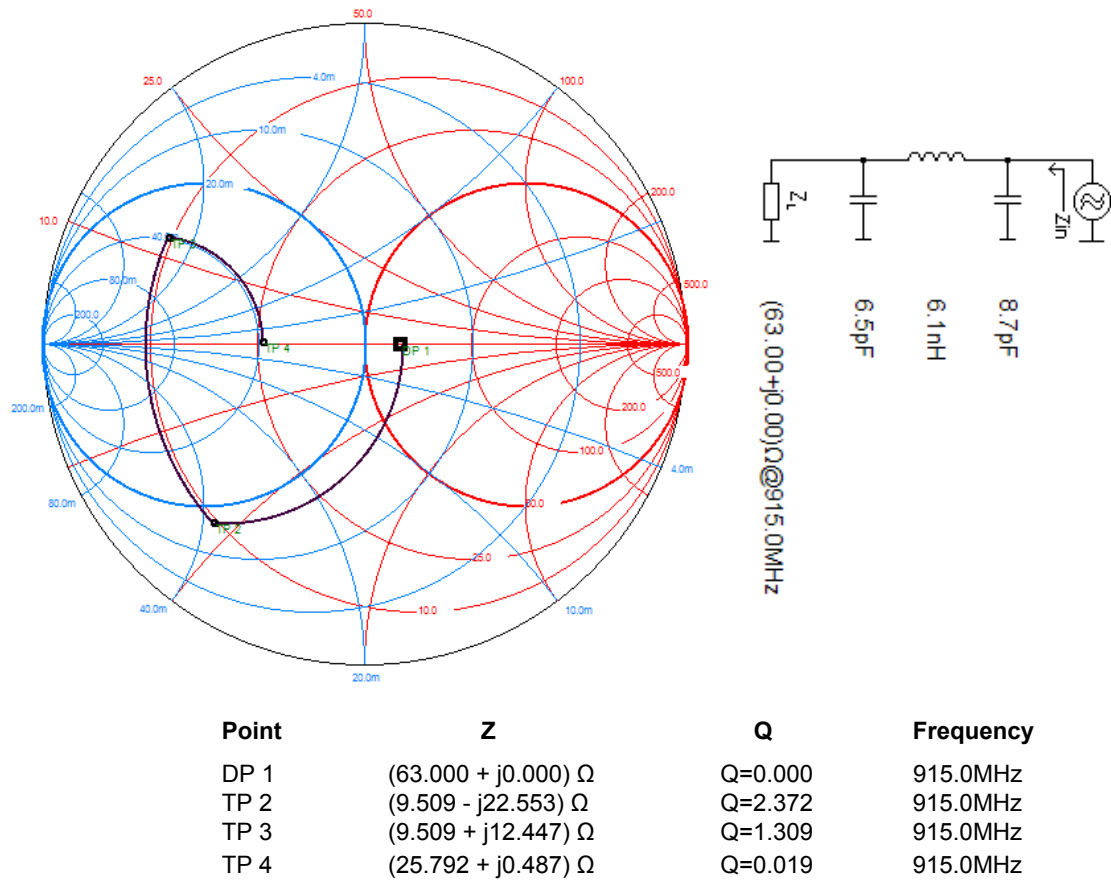


Figure 2.8. TX Match Process Demonstrated at 915 MHz with One-half of the Differential Network

**Note:** In the figure above, the half Pi network matches the  $50/2 = \sim 25 \Omega$  to  $Z_{load}/2 = \sim 63 \Omega$ .


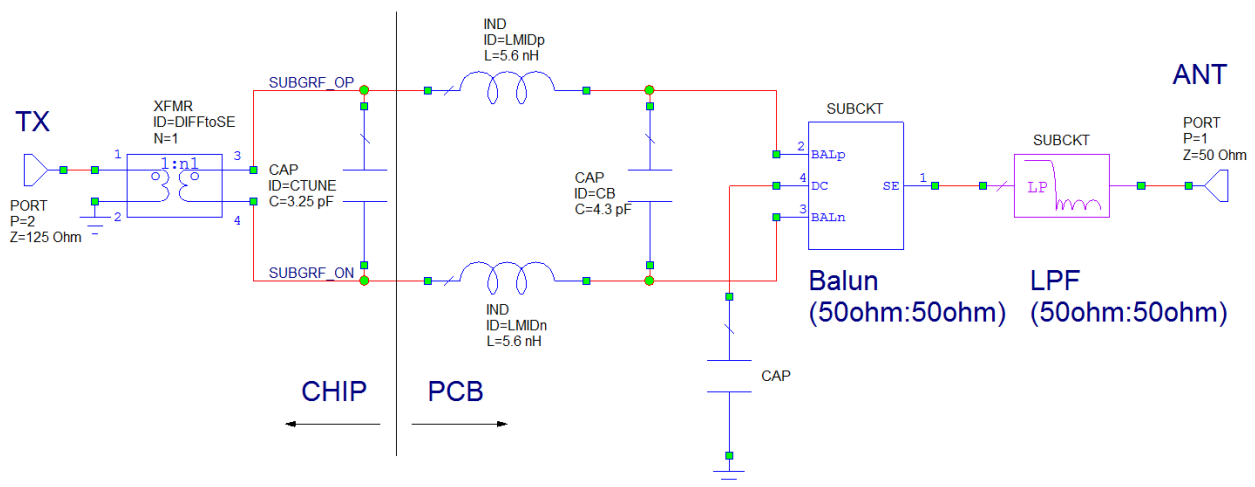


Figure 2.9. TX Match for  $Z_{load} = 125 \Omega$  at 915 MHz

The simulated differential load impedance for this network is shown below, and is very close to the desired target value of 125  $\Omega$ . Note that the Smith Chart has also been normalized here to  $Z_0 = 125 \Omega$ .

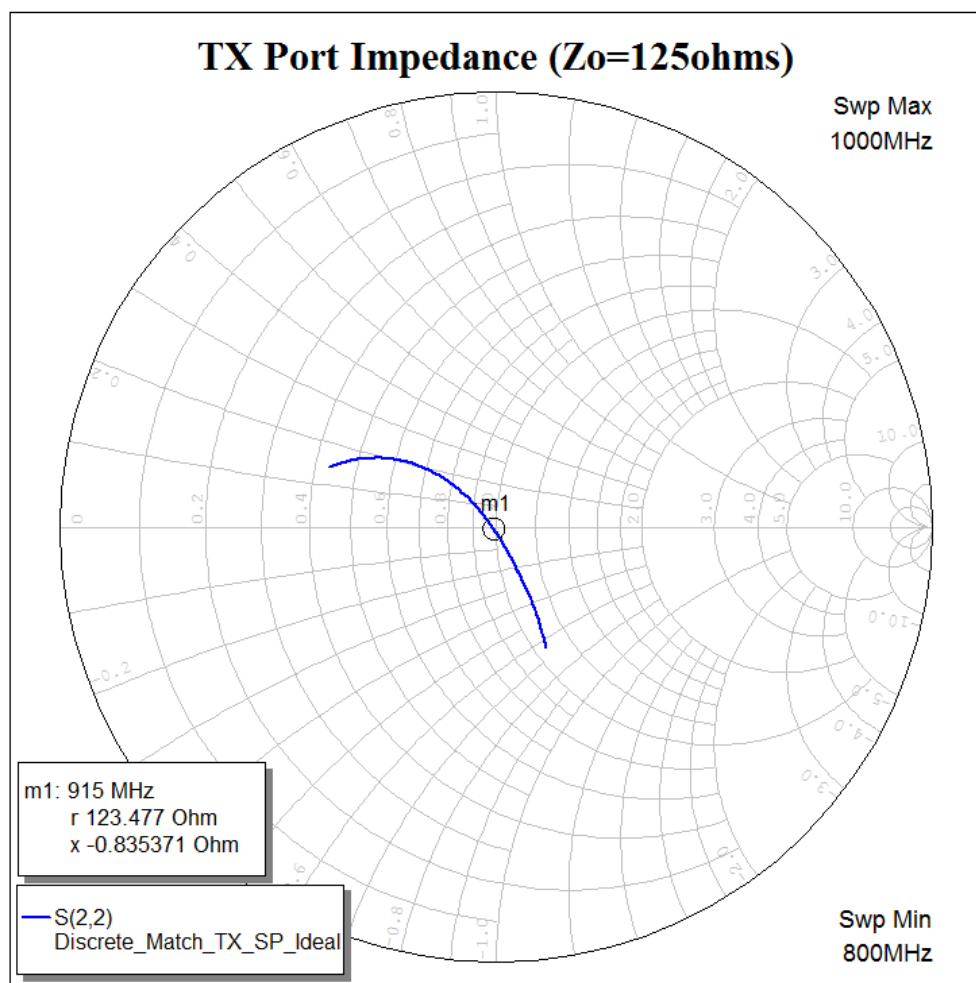

**Figure 2.10. Differential TX Load Impedance at 915 MHz**

If the user desires a TX-only application, the match topology of [Figure 2.9 TX Match for  \$Z\_{load} = 125 \Omega\$  at 915 MHz on page 11](#) is sufficient. A boundary line has been drawn in this plot to clearly show those components which lie outside the RFIC.

## 2.4.2 RX Signal Path and Match

The RX signal path makes use of all of the TX signal path and match presented in the previous section. The RX signal path “taps off” the end of the TX match and additionally provides a differential series-C, shunt-L impedance transformation network (refer back to [Figure 2.6 Impedance Transformation Block Topology on page 8](#)).

The differential RX input impedance of the EFR32 family of chips is very high, as shown in the Smith Chart admittance plot in the figure below. The RX input may be approximated by an equivalent circuit consisting of a high-value resistance ( $\sim 5\text{ k}\Omega$  to several  $10\text{'s}$  of  $\text{k}\Omega$ ) in parallel with a small capacitance ( $\sim 0.76\text{ pF}$  to  $\sim 1\text{ pF}$ ), with the values varying somewhat as a function of frequency.

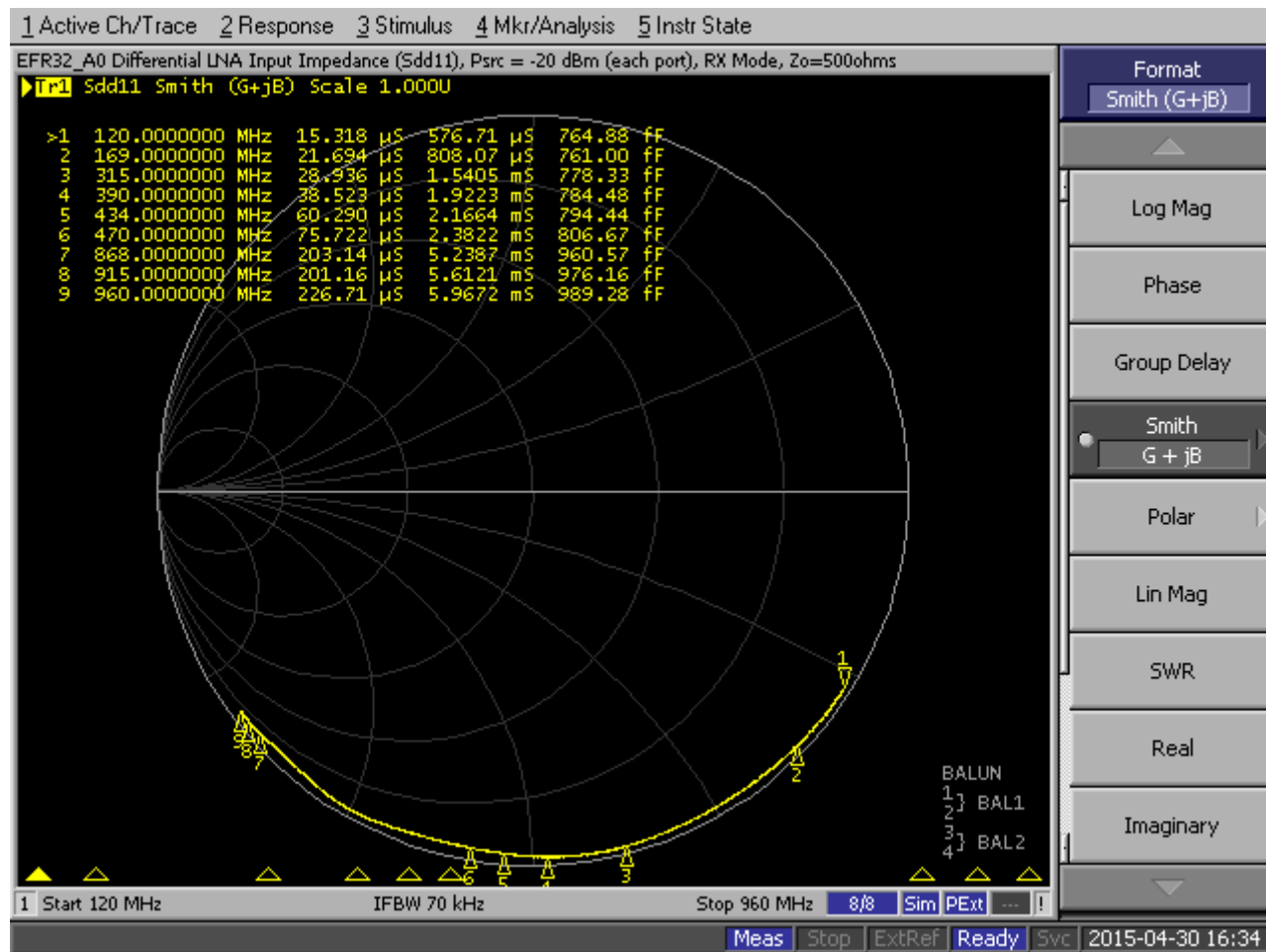


Figure 2.11. EFR32 Differential RX Input Admittance

Due to the high value of equivalent parallel resistance (~5 kΩ at 915 MHz), Silicon Labs makes no attempt to construct a true complex conjugate match at the RX interface. Such an extreme impedance transformation ratio (e.g., ANT=50 Ω to RX=5000 Ω) would require an extremely high-Q, narrowband, and difficult-to-tune matching network. The LNA circuitry acts more as a voltage amplifier than a power amplifier, and thus less emphasis is placed on maximum power transfer to the LNA input and more emphasis is placed on the passive voltage gain of the RX matching network. A large value of passive voltage gain in the match network, prior to the active circuitry of the LNA, helps suppress the 2<sup>nd</sup>-stage contributions of noise from the LNA and downstream circuits, as expressed in Friis' Equation:

$$F_{TOTAL} = F_1 + \left( \frac{F_2 - 1}{G_1} \right)$$

Equation 2

The concept of passive voltage gain is simple: if a lossless network is used to accomplish an impedance transformation (from Z<sub>1</sub> to Z<sub>2</sub>), the power gain (or loss) through the network is zero, but the voltage at the terminals of the network are different. If Z<sub>2</sub> > Z<sub>1</sub>, then mathematically,

$$Z_2 \left( = \frac{V_2}{I_2} \right) > Z_1 \left( = \frac{V_1}{I_1} \right) \rightarrow V_2 > V_1$$

Equation 3

Referring back to [Figure 2.6 Impedance Transformation Block Topology on page 8](#), the impedance transformation ratio of the RX portion of the match (and thus its passive voltage gain) is set by the LGATE:CSER ratio. This is demonstrated using the simple AC test bench of the figure below, in which the LGATE:CSER ratio is swept while maintaining (approximately) a constant LGATE\*CSER product. The resulting AC voltage gain curves are shown in [Figure 2.13 RX Passive Voltage Gain vs LGATE:CSER Ratio on page 15](#).

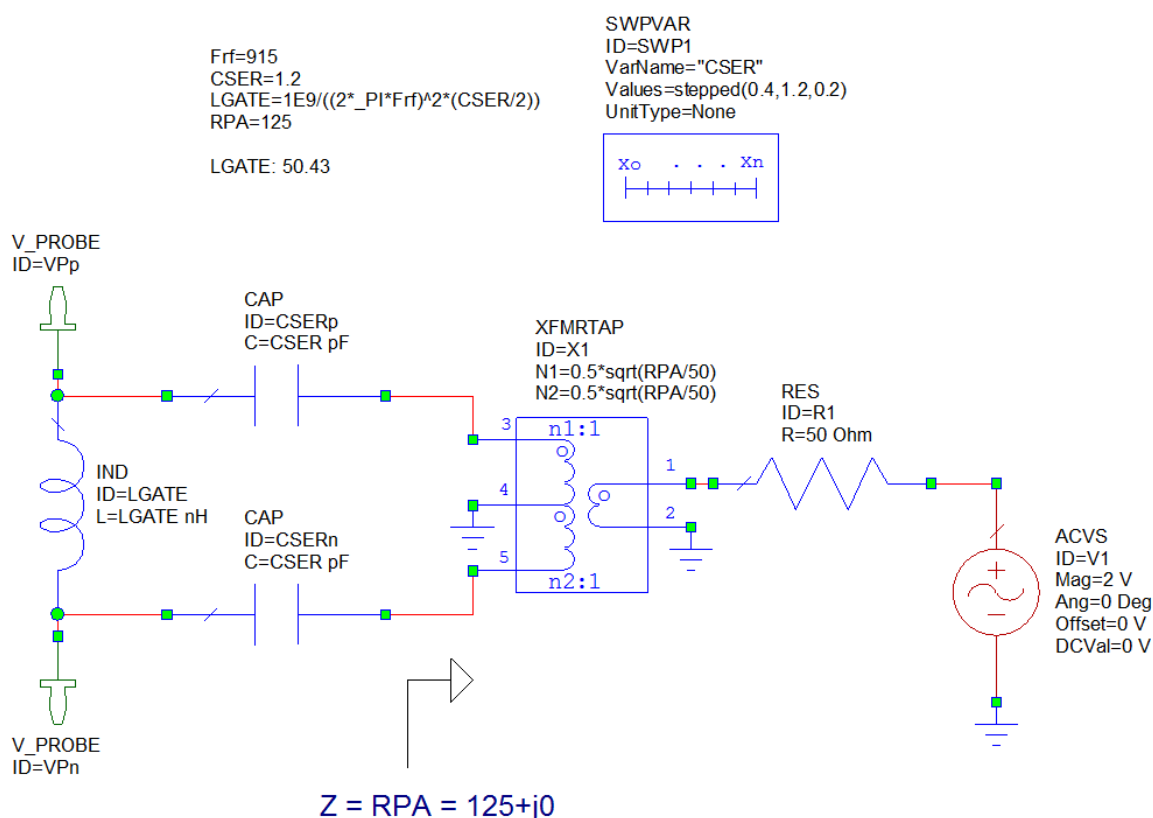


Figure 2.12. RX Gain Test Bench

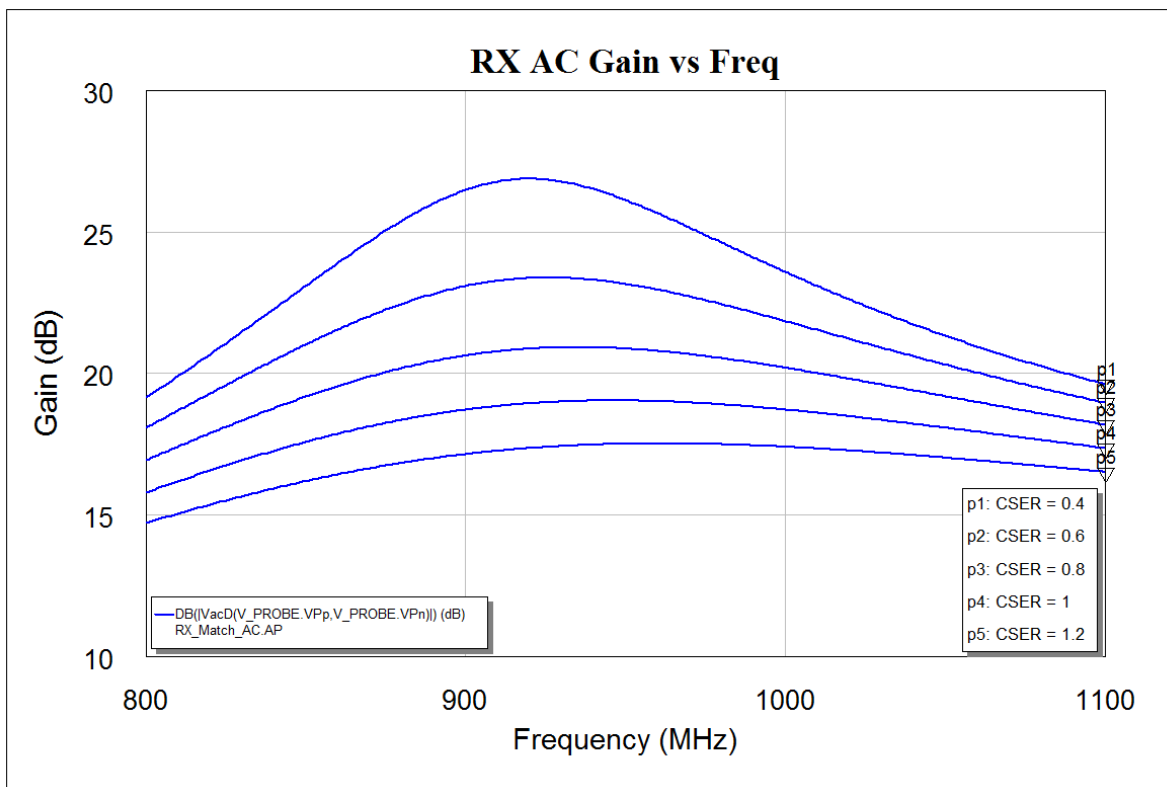


Figure 2.13. RX Passive Voltage Gain vs LGATE:CSER Ratio

The reader is cautioned against designing for extremely large values of RX voltage gain through use of very large LGATE:CSER ratios. The resulting design may have a very narrowband frequency response and may be difficult to tune due to the very small value of capacitance and/or large value of inductance. Additionally, the finite Q-factor of the inductor (as well as the input resistance of the LNA) will limit the maximum achievable gain (an effect not shown in the ideal simulation of [Figure 2.13 RX Passive Voltage Gain vs LGATE:CSER Ratio on page 15](#)). For this reason, use of a high-quality inductor (i.e., wire-wound inductor) is recommended for LGATE.


As shown in the admittance plot of [Figure 2.11 EFR32 Differential RX Input Admittance on page 13](#), the differential RX input of the EFR32 family of chips may be viewed as a large-value resistance in parallel with a small-value capacitance. A more accurate representation of the RX match is shown in [Figure 2.14 RX Match \(Including RLNA and CLNA\) on page 16](#). This schematic demonstrates that while only one discrete parallel inductance (LGATE) is used in the actual match, it may be viewed as consisting of two inductors in parallel, where

$$L_{GATE} = L_{LNA} \parallel L_{SH}$$

Equation 4

The LLNA component of the inductance parallel-resonates with CLNA at the desired frequency of operation and effectively cancels it, leaving the LSH component of inductance to work with CSER to accomplish the RX impedance transformation and passive voltage gain.



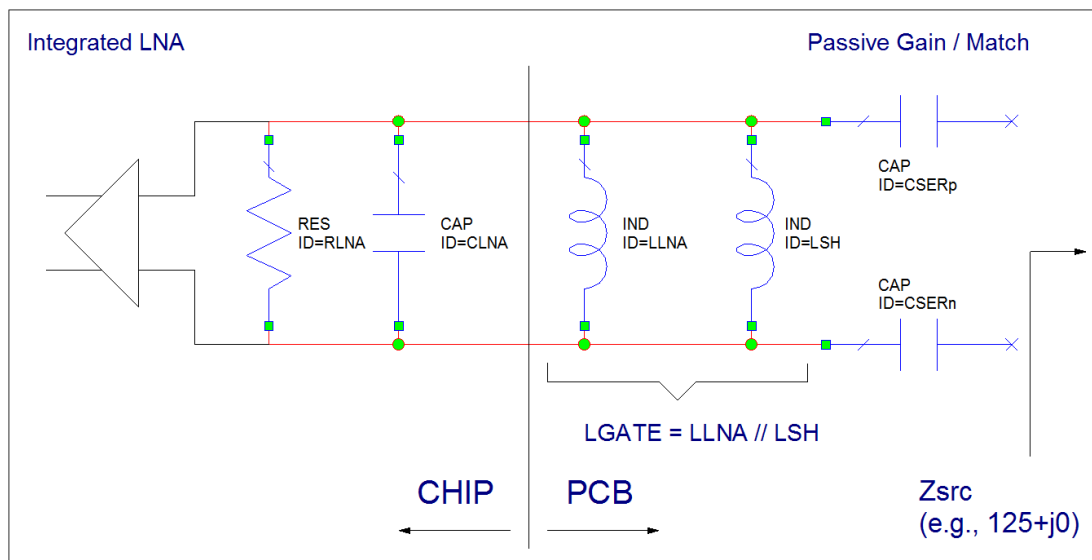

**Figure 2.14. RX Match (Including RLNA and CLNA)**

Although not demonstrated here, it may be shown that the overall frequency response of the RX match becomes more narrowband as the value of CLNA is increased. As the total value of CLNA is the sum of LNA input capacitance plus parasitic capacitance from PCB traces and pads, it is thus to the designer's advantage to minimize CLNA through optimization of the PCB layout. The value of CLNA (0.76pF to 0.99pF, as a function of frequency) shown in the admittance plot of [Figure 2.11 EFR32 Differential RX Input Admittance on page 13](#) represents its minimum possible value, as the measurement was taken with all PCB traces and pads removed and thus represents the value of the LNA input capacitance by itself. A value of CLNA = 1.0 pF is reasonable for highly-optimized board layouts, while a value of CLNA = 1.25 pF may be appropriate for less-optimal board layouts.

Just as there was no single, unique solution for the CB-LMID-CTUNE TX impedance transformation path (refer to [Figure 2.9 TX Match for Zload = 125 Ω at 915 MHz on page 11](#)), there is also no unique solution for LGATE and CSER in the RX matching path. As discussed above, the designer may (within reasonable limits) adjust the LGATE:CSER ratio to trade off the bandwidth of the RX frequency response for the transformed RX impedance and magnitude of passive voltage gain. Given the value of CLNA, it is a simple matter to calculate the inductance LLNA required to parallel-resonate CLNA at the desired frequency of operation:

$$L_{LNA} = \frac{1}{\omega_{RF}^2 \cdot C_{LNA}}$$

**Equation 5**

Continuing the design example at 915 MHz with CLNA = 1.0 pF, the calculated value of LLNA = 30.25 nH.

The calculation of LSH is unfortunately not as simple. A reasonable target LGATE:CSER ratio must first be selected using a combination of simulation, bench experience, or guidance from Silicon Labs (as provided within this application note). A trial value of CSER is next selected as the starting point for the remaining calculations. For the design example at 915 MHz, Silicon Labs states that CSER = 1.8 pF is a reasonable selection.

The value of LSH that resonates with CSER is subsequently calculated. As the two CSER capacitors in the differential RX match of [Figure 2.14 RX Match \(Including RLNA and CLNA\) on page 16](#) are effectively in series with LSH (after cancellation of CLNA by LLNA), it would at first glance seem that the required value of LSH is simply that which resonates with 0.5 x CSER at the desired frequency of operation. However, this is not correct; it neglects the effect of ZSRC upon the resonance of the circuit.

The two CSER capacitors appear in series with the source resistance, i.e., the transformed impedance resulting from the TX portion of the match. Continuing the design example at 915 MHz, this was  $Z_{SRC} = Z_{TX} = \sim 125 + j0 \, \Omega$  (refer back to [Figure 2.9 TX Match for Zload = 125  \$\Omega\$  at 915 MHz on page 11](#) and [Figure 2.10 Differential TX Load Impedance at 915 MHz on page 12](#)). Prior to calculation of the value for LSH, it is first necessary to transform this series R-C network into an equivalent parallel R-C network. Mathematically,

$$Q = \frac{1}{R_{SRC} * \omega_{RF} * (0.5 * C_{SER})}$$

Equation 6

$$C_{SER-SH} = \frac{0.5 * C_{SER}}{1 + \left(\frac{1}{Q}\right)^2}$$

Equation 7

$$L_{SH} = \frac{1}{\omega_{RF}^2 * C_{SER-SH}}$$

Equation 8

Continuing the design example at 915 MHz with  $R_{SRC} = 125 \, \Omega$  and  $C_{SER} = 1.8 \, \text{pF}$ , this results in  $LSH = 47.68 \, \text{nH}$ . It is then a simple matter to use Equation 4 to determine the value of  $LGATE = 18.51 \, \text{nH}$ .

The values shown in the table below represent one possible set of solutions for RX matching component values, assuming  $CLNA = 1.0 \, \text{pF}$  and  $R_{SRC} = 125 \, \Omega$ . As mentioned previously, this is not a unique set of solutions. For example, if the value of  $C_{SER}$  had been chosen instead as  $C_{SER} = 1.2 \, \text{pF}$ , the calculated required value for  $LGATE$  at 915 MHz would be  $20.09 \, \text{nH}$ . Both solutions easily provide acceptable performance

Alternatively, if the assumed value of  $CLNA$  had been increased to  $CLNA = 1.25 \, \text{pF}$  (i.e., due to increased trace and pad parasitics), one possible solution at 915 MHz would be calculated as  $C_{SER} = 0.9 \, \text{pF}$  and  $LGATE = 18.25 \, \text{nH}$ .

The deciding factor in choosing one solution over another is often how close the calculated component values fall near standard tolerance values (e.g., 5% tolerance parts).

Table 2.3. Example LGATE:CSER Calculations vs Frequency ( $R_{SRC}=125 \, \Omega$ )


Freq	$C_{SER}$	Q	$C_{LNA}$	$L_{LNA}$	$L_{SH}$	$L_{GATE}$
915 MHz	1.8 pF	1.546	1.0 pF	30.25 nH	47.68 nH	18.51 nH
868 MHz	1.6 pF	1.834	1.0 pF	33.62 nH	54.53 nH	20.80 nH
490 MHz	1.6 pF	3.248	1.0 pF	105.5 nH	144.4 nH	60.96 nH
434 MHz	1.6 pF	3.667	1.0 pF	134.5 nH	180.6 nH	77.08 nH
315 MHz	1.8 pF	4.491	1.0 pF	255.3 nH	297.7 nH	137.4 nH
170 MHz	3.0 pF	4.993	1.0 pF	876.5 nH	607.8 nH	358.9 nH

### 2.4.3 Interaction of TX and RX Signal Paths

To this point, there has been no discussion of how the TX and RX signal paths may be directly tied (as shown in [Figure 2.6 Impedance Transformation Block Topology on page 8](#)) while still “playing nicely” together. That topic is now considered.

The TX signal path and match heavily influences the RX performance, while the RX signal path and match only weakly affects the TX performance. The recommended design approach is therefore to construct the match for the TX path first, followed by the addition of the RX match.

The PA output impedance of the EFR32 family chips may be viewed as a moderate-value resistance (500 to 1000  $\Omega$ ) in parallel with the integrated CTUNE tuning capacitor. The value of the PA equivalent parallel output resistance varies somewhat depending upon whether the PA circuit is enabled or disabled (i.e., TX or RX mode). However, the variation is not large, and as the PA output resistance is typically several times larger than the desired PA load impedance (e.g., 125  $\Omega$ ), it may be ignored in the matching process as a first-order approximation. That is to say, the source resistance seen by the RX match (CSER and LGATE, as seen in [Figure 2.14 RX Match \(Including RLNA and CLNA\) on page 16](#)) is primarily determined by the TX match (CB, LMID, and CTUNE).

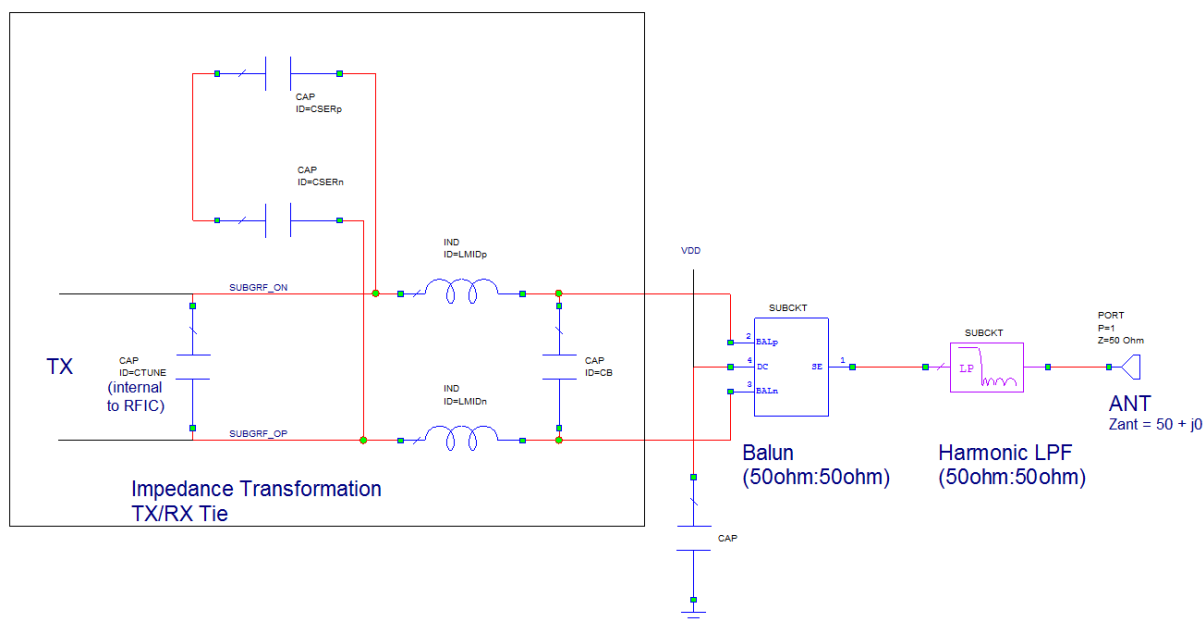

**Figure 2.15. Effective Matching Network in TX Mode**

The RX match, however, does provide a small additional load on the TX signal path. As shown in [Figure 2.2 General Topology of sub-GHz RF Match on page 3](#), a switch is integrated inside the EFR32 chip across the RX input pins. The switch is open while in RX mode but closed in TX mode, thus shorting the RX input pins together and shorting across CLNA and LGATE. This effectively places the two CSER capacitors in series with one another, and in parallel across the TX pins, as shown in [Figure 2.5 Typical Performance through LPF + Balun \(915 MHz, N = 5, 0900BL15C050 Balun\) on page 7](#). In this fashion, the effective value of the CTUNE tuning capacitor is increased by approximately  $0.5 \times$  CSER while in TX mode.

This switch helps isolate the TX and RX signal paths, and attenuates the amplitude of the TX signal swing that is observed across the RX input pins.

### 3. Putting it All Together

The previous sections have discussed the design procedures for each of the sub-blocks (lowpass filter, balun, and impedance transformation network) of the complete match. The topology of the entire discrete matching network for an application at 868 MHz or 915 MHz is shown in [Figure 2.6 Impedance Transformation Block Topology on page 8](#). The topology of the matching network for applications in lower frequency bands is shown in [Figure 2.7 TX Impedance Transformation Network on page 10](#).

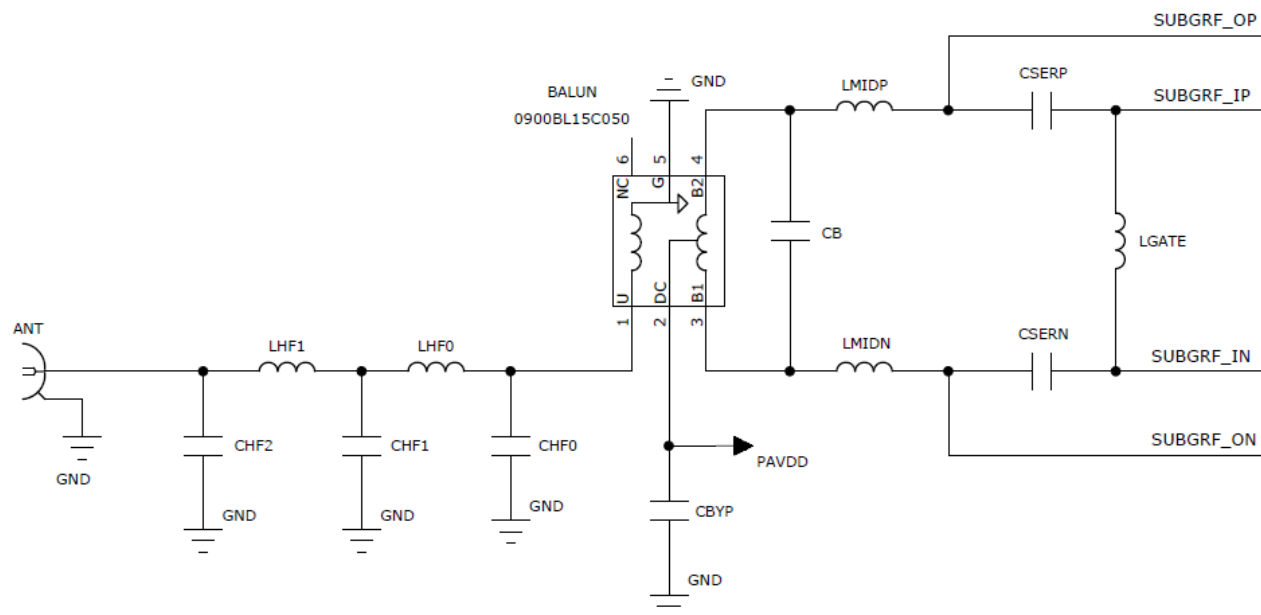


Figure 3.1. Complete Match Network Topology for 868 M/915 M

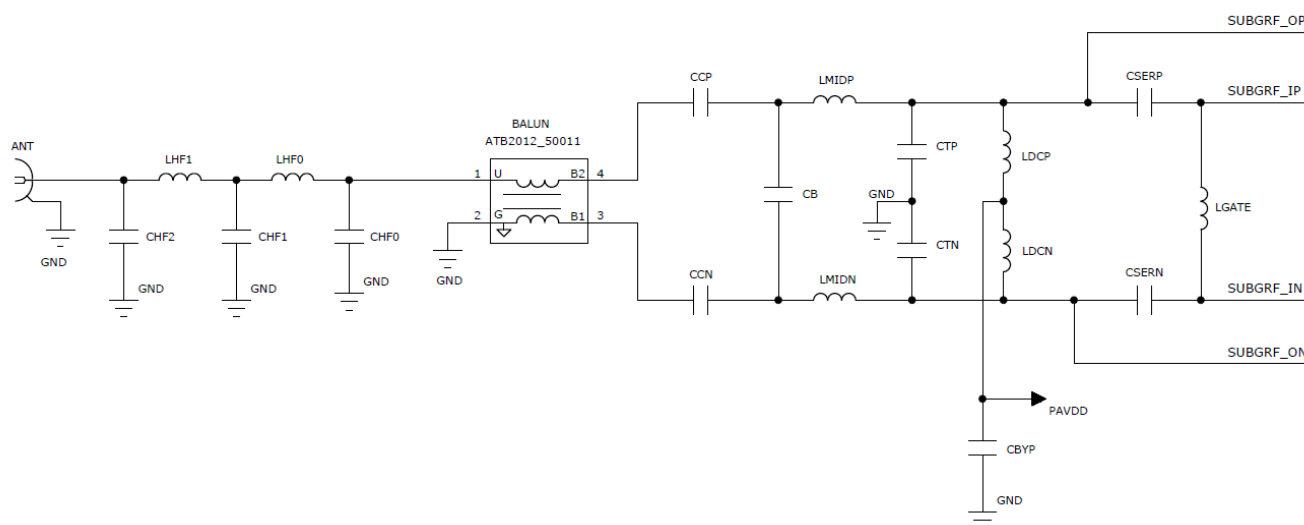


Figure 3.2. Complete Match Network Topology for 169 M/315 M/434 M/490 M

The high-band and the low-band matching topologies differ in the following respects:


- The low-band match includes pull-up inductors LDCP and LDCN, as a suitable balun with center tap (for the DC feed function) was not identified by Silicon Labs for use in low-band applications. These inductors should be high-value (e.g., 470 nH) with low DC winding resistance (e.g., Murata LQW18CNR47).
- The low-band match includes DC blocking capacitors CCP and CCN. The balun selected by Silicon Labs for use in low-band applications provides DC continuity between the primary and secondary windings, and thus DC blocking capacitors must be used else VDD will be shorted to ground through the balun. These capacitors may be removed if a balun with no DC continuity between windings is selected. The value of the capacitors should be selected to provide very low AC impedance while remaining below the series-resonant frequency of the capacitor.
- The low-band match includes provisions for additional tuning capacitors CTP and CTN. These additional capacitors will likely be needed only for applications at  $\leq 315$  MHz. At such low frequencies, the range of the internal PA tuning capacitor CTUNE may not be sufficient and may need to be augmented by these external discrete capacitors.
- The low-band match applies 7<sup>th</sup>-order filter at some bands.

The reader may desire to use the equations and design process discussed within this application note to construct an entirely new match. However, many other readers may simply desire a tabulated list of component values for matches and applications already developed by Silicon Labs. For these readers, the following tables are provided.

The component values required for the various lowpass filter section(s) were previously summarized in [Table 2.1 Lowpass Filter Component Values vs. Frequency on page 5](#), and are not reproduced here in the interest of brevity. To date, Silicon Labs has used two different baluns, depending upon the frequency of the application. The 0900BL15C050 balun from Johanson Technology (JTI) has been used for high-band designs (868M/915M/950M0, while the ATB2012\_50011 balun from TDK has been used in all other designs.

As discussed in [2.4.2 RX Signal Path and Match](#), the value of CLNA has an effect upon the component values in the RX section of the match (e.g., CSER and LGATE). The optimized layouts used by the Silicon Labs reference designs and also described in "AN928: EFR32 Layout Design Guide" has quite low PCB parasitics between the RX pins and thus, the matching element values can be calculated assuming CLNA=1pF. The element values for this case is summarized in [Table 3.1 Summary of Matching Component Values vs. Frequency \(CLNA = 1.0 pF\) on page 21](#). The last column shows, whether the match is already bench tuned and tested or not. The tested boards are fully characterized by Silicon Labs. The not tested matches can be used as a starting point for bench evaluation.

In the Silicon Labs reference design layouts the ground metallization of the inner PCB layers are eliminated beneath the RX match area to reduce the parasitic capacitance between the RX pins, as shown in the figure below. The CLNA = 1 pF value can be maintained only with this trick.

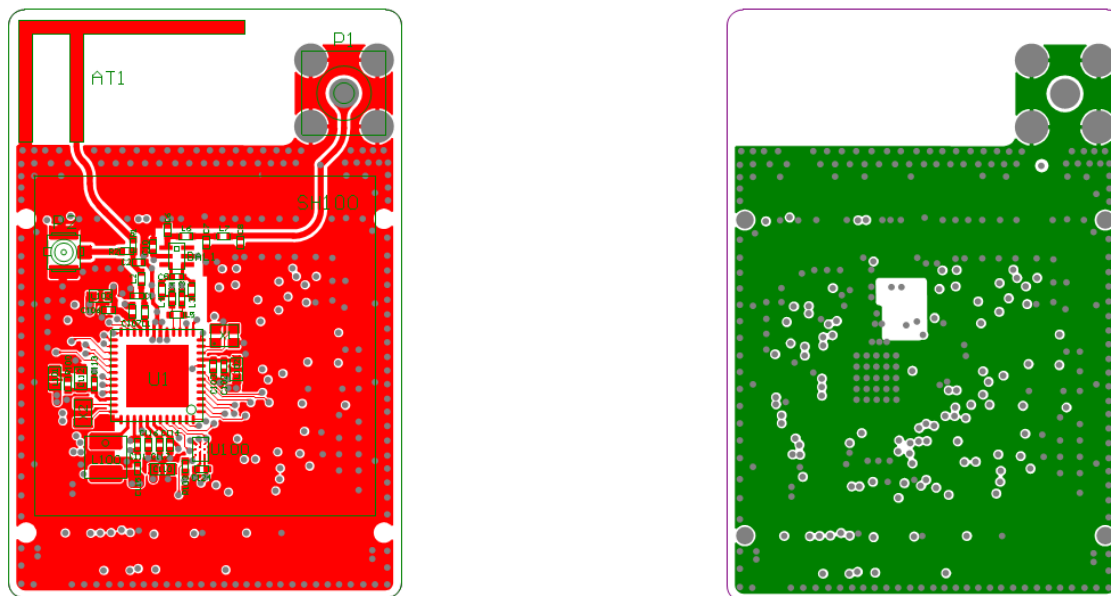

**Figure 3.3. Elimination of the GND Metallization in the Inner Layers Beneath the RX Match Area**

If the inner layer metallization cannot be eliminated due to any reason the CLNA increases and will be close to 1.25pF. The corresponding component values for CLNA=1.25pF case are summarized in [Table 3.2 Summary of Matching Component Values vs. Frequency \(CLNA = 1.25 pF\) on page 22](#) below. Unfortunately, these match values were not bench tested yet. In simulations they yield slightly worse RF performances (lower TX powers, worse sensitivities, and narrower bandwidths).

As an example the final schematic of the 868 MHz/2.4 GHz and 169MHz /2.4 GHz dual band boards are given in [Appendix 1. Schematics](#).

The measured result of the tested boards in TX mode are summarized in [Table 3.3 Summary of Matching RF performance in TX mode \(CLNA = 1.0 pF\) on page 22](#). In RX mode the sensitivity data given in the datasheet are valid for all matches.

**Table 3.1. Summary of Matching Component Values vs. Frequency (CLNA = 1.0 pF)**

Freq Band	P <sub>OUT</sub>	PAVDD	LGATE	CSER	LMID	CB	CT	LDC	BALUN	LPF	Tested
169 MHz	20 dBm	3.3 V	390 nH	3.0 pF	36 nH	10 pF	13 pF	470 nH	TDK	N = 7	Y
	10 dBm	1.7 V	390 nH	3.0 pF	51 nH	12 pF	10 pF	470 nH	TDK	N = 3	Y
315 MHz	14 dBm	1.8 V	120 nH	2.7 pF	18 nH	3.9 pF	3.3 pF	470 nH	TDK	N = 7	Y
434 MHz	14 dBm	1.8 V	75 nH	1.8 pF	13 nH	2.7 pF	N/A	470 nH	TDK	N = 5	Y
	10 dBm	1.7 V	75 nH	1.6 pF	18 nH	4.7 pF	N/A	470 nH	TDK	N = 5	Y
490 MHz	20 dBm	3.3 V	62 nH	1.6 pF	9.1 nH	3.3pF	N/A	470 nH	TDK	N = 5	Y
868 MHz	20 dBm	3.3 V	18 nH	1.9 pF	3.3 nH	3.9 pF	N/A	N/A	JTI	N = 5	Y
	14 dBm	1.8 V	18 nH	1.9 pF	3.3 nH	3.9 pF	N/A	N/A	JTI	N = 5	Y
915 MHz	20 dBm	3.3 V	18 nH	1.8 pF	3.3 nH	3.9 pF	N/A	N/A	JTI	N = 5	Y
	13 dBm	1.7 V	18 nH	1.8 pF	3.3 nH	3.9 pF	N/A	N/A	JTI	N = 3	N
950 MHz	13 dBm	1.7 V	TBD	TBD	TBD	TBD	N/A	N/A	JTI	N = 3	N

**Table 3.2. Summary of Matching Component Values vs. Frequency (CLNA = 1.25 pF)**

Freq Band	P <sub>OUT</sub>	PAVDD	LGATE	CSER	LMID	CB	CT	LDC	BALUN	LPF	Tested
169 MHz	20 dBm	3.3 V	330 nH	3.0 pF	36 nH	10 pF	13 pF	470 nH	TDK	N = 7	N
	10 dBm	1.7 V	330 nH	3.0 pF	43 nH	12 pF	11 pF	470 nH	TDK	N = 3	N
315 MHz	14 dBm	1.8 V	120 nH	1.8 pF	22 nH	5.1 pF	2.7 pF	470 nH	TDK	N = 5	N
434 MHz	14 dBm	1.8 V	75 nH	1.0 pF	15 nH	2.7 pF	N/A	470 nH	TDK	N = 5	N
	10 dBm	1.7 V	75 nH	1.0 pF	18 nH	3.0 pF	N/A	470 nH	TDK	N = 3	N
490 MHz	20 dBm	3.3 V	62 nH	1.0 pF	9.1 nH	3.3 pF	N/A	470 nH	TDK	N = 5	N
868 MHz	20 dBm	3.3 V	20 nH	0.9 pF	4.3 nH	4.7 pF	N/A	N/A	JTI	N = 5	N
	14 dBm	1.8 V	20 nH	0.9 pF	4.7 nH	4.7 pF	N/A	N/A	JTI	N = 5	N
915 MHz	20 dBm	3.3 V	18 nH	0.9 pF	3.9 nH	4.3 pF	N/A	N/A	JTI	N = 5	N
	13 dBm	1.7 V	18 nH	0.9 pF	3.9 nH	4.3 pF	N/A	N/A	JTI	N = 3	N
950 MHz	13 dBm	1.7 V	TBD	TBD	TBD	TBD	N/A	N/A	JTI	TBD	N

**Table 3.3. Summary of Matching RF performance in TX mode (CLNA = 1.0 pF)**

Freq Band	P <sub>OUT_GOAL</sub>	PAVDD	Pfund	P <sub>2<sup>nd</sup></sub>	P <sub>3<sup>rd</sup></sub>	I <sub>pa</sub>
169 MHz	20 dBm	3.3 V	19.9 dBm	–58 dBm	–62 dBm	76 mA
	10 dBm	1.7 V	10 dBm	–59 dBm	–47 dBm	14 mA
315 MHz	14 dBm	1.8 V	14 dBm	–59 dBm	–66 dBm	39.6 mA
434 MHz	14 dBm	1.8 V	14.1 dBm	–55 dBm	–60 dBm	37.3 mA
	10 dBm	1.7 V	10 dBm	–62 dBm	–66 dBm	14.7 mA
490 MHz	20 dBm	3.3 V	19.9 dBm	–57 dBm	–62 dBm	77 mA
868 MHz	20 dBm	3.3 V	19.9 dBm	–32 dBm	–64 dBm	85 mA
	14 dBm	1.8 V	14 dBm	–45 dBm	–70 dBm	40.5 mA
915 MHz	20 dBm	3.3 V	20.1 dBm	–34 dBm	–51 dBm	86 mA
	13 dBm	1.7 V	TBD	TBD	TBD	TBD
950 MHz	13 dBm	1.7 V	TBD	TBD	TBD	TBD

## Appendix 1. Schematics

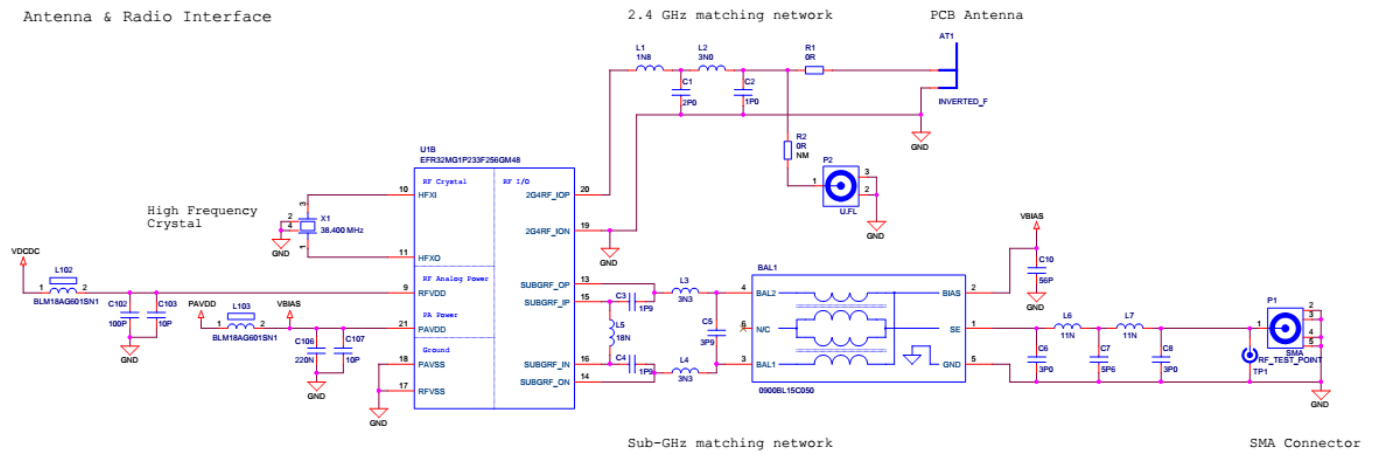


Figure 1.1. 868 MHz / 2.4 GHz Dual Band Board Schematic


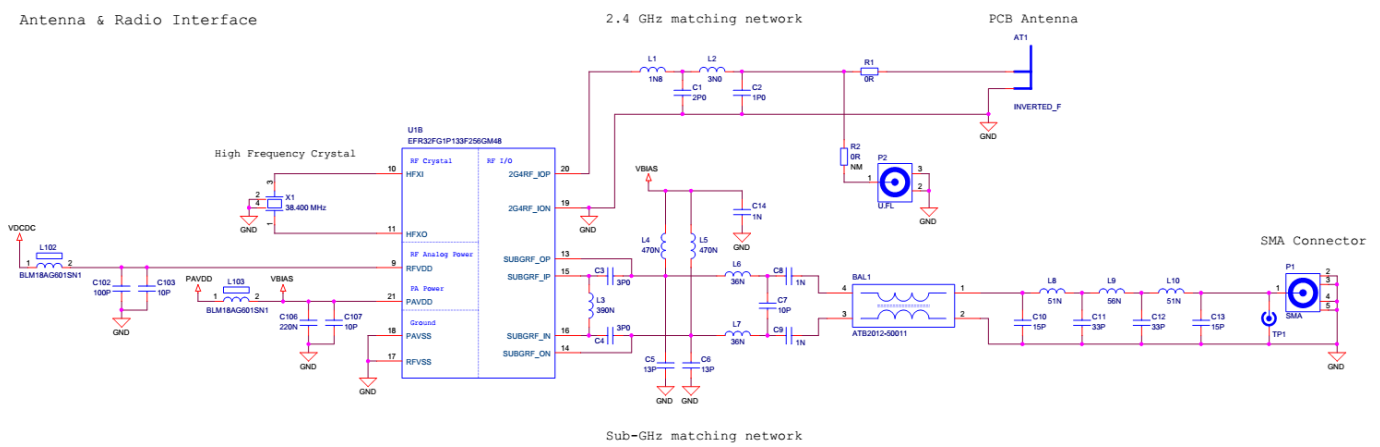


Figure 1.2. 169 MHz / 2.4 GHz Dual Band Board Schematic

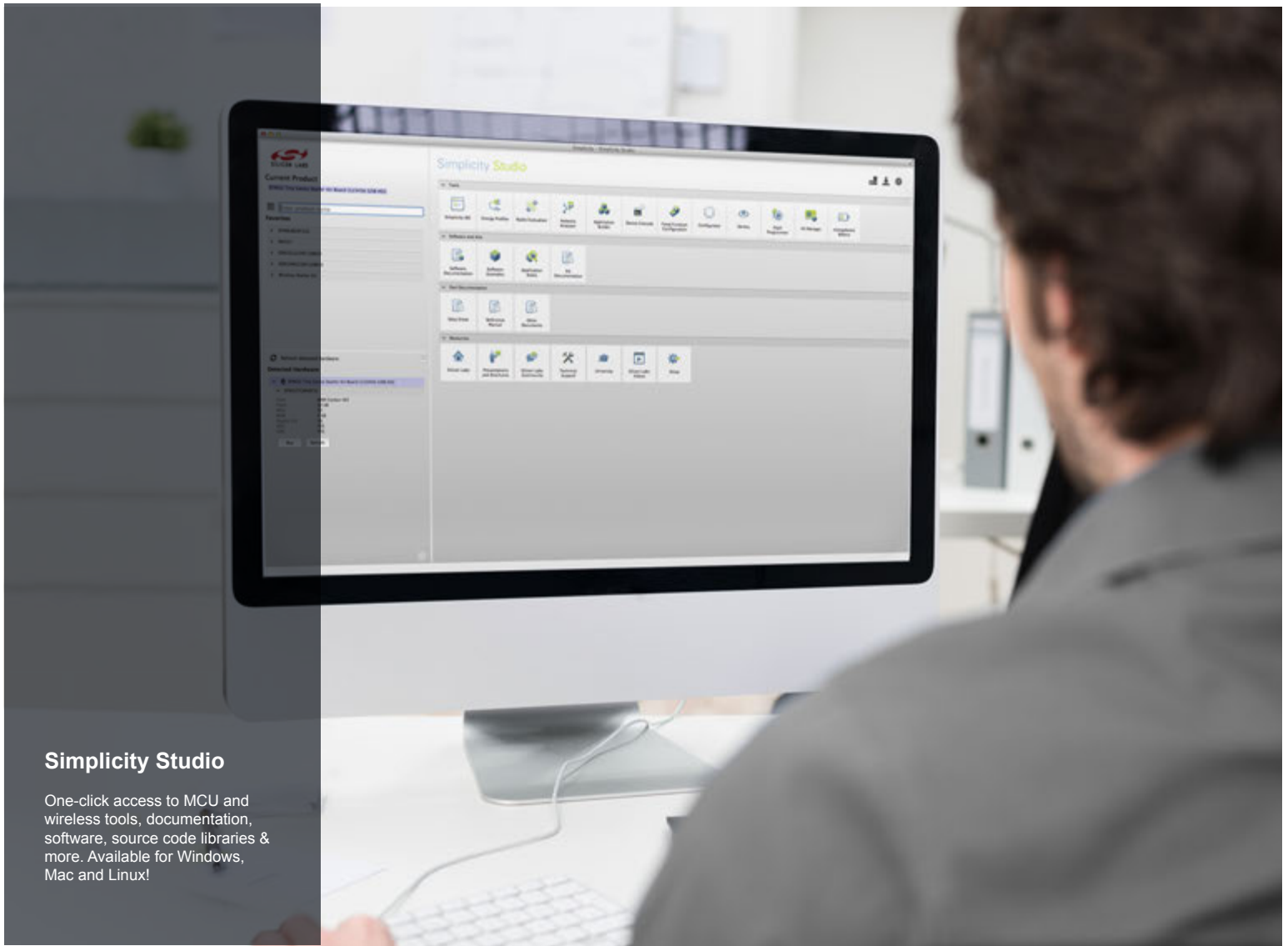



## Simplicity Studio

One-click access to MCU and wireless tools, documentation, software, source code libraries & more. Available for Windows, Mac and Linux!



**IoT Portfolio**  
[www.silabs.com/IoT](http://www.silabs.com/IoT)



**SW/HW**  
[www.silabs.com/simplicity](http://www.silabs.com/simplicity)



**Quality**  
[www.silabs.com/quality](http://www.silabs.com/quality)



**Support and Community**  
[community.silabs.com](http://community.silabs.com)

### Disclaimer

Silicon Laboratories intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Laboratories products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Laboratories reserves the right to make changes without further notice and limitation to product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Silicon Laboratories shall have no liability for the consequences of use of the information supplied herein. This document does not imply or express copyright licenses granted hereunder to design or fabricate any integrated circuits. The products are not designed or authorized to be used within any Life Support System without the specific written consent of Silicon Laboratories. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Laboratories products are not designed or authorized for military applications. Silicon Laboratories products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons.

### Trademark Information

Silicon Laboratories Inc.®, Silicon Laboratories®, Silicon Labs®, SiLabs®, and the Silicon Labs logo®, Bluegiga®, Bluegiga Logo®, Clockbuilder®, CMEMS®, DSPLL®, EFM®, EFM32®, EFR®, Ember®, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZRadio®, EZRadioPRO®, Gecko®, ISOModem®, Precision32®, ProSLIC®, Simplicity Studio®, SIPHY®, Telegesis, the Telegesis Logo®, USBXpress® and others are trademarks or registered trademarks of Silicon Laboratories Inc. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Keil is a registered trademark of ARM Limited. All other products or brand names mentioned herein are trademarks of their respective holders.



Silicon Laboratories Inc.  
 400 West Cesar Chavez  
 Austin, TX 78701  
 USA

<http://www.silabs.com>